

Low Voltage Devices in the Real World

Prepared by: Fred Zlotnick
ON Semiconductor



ON Semiconductor™

<http://onsemi.com>

TECHNICAL NOTE

Many microprocessor and DSPs need to operate at very low Voltage, in order to conserve power and not over-dissipate. Issues arise when the designer has a device like a DSP operating at 1.6 Volts and needs to interface with other semiconductors operating at 3 Volts or more.

The problem stems from the output of the DSP only pulling up to its supply voltage. For nearly all CMOS devices, the a logic level high (V_{IH}) is guaranteed to be 70% of V_{CC} , and logic level low (V_{IL}) is 30% of. If a DSP/MCU is operating at 1.6 Volts, a no-load output can be guaranteed to $V_{CC} - 0.2$ V, so the output will be ≈ 1.5 Volts. This level of output cannot match a 3.0 V CMOS device, e.g. ASIC. The DSP/MCU simply cannot pull up high enough.

Solutions: ON Semiconductor has many different gates, buffers, inverters that are called "T" versions in the VHC family. The VHC family is a 0.6 μ m CMOS family of single gate, and multigate devices. They offer good speed and low cost. We offer many devices available in the single gate family. The "T" version VHC devices are full/Low Voltage TTL compatible when operating at 5.0 Volts, however, ON Semiconductor has fully characterized its VHCT family at 3.0 Volts as well. VHC/VHCT is considered to be a transitional family, providing logic, buffering and switching, either to a lower or higher voltage.

Translation of the output of a low Voltage device (1.6 to 2.0 V) to 3.0 V or higher requires some sort of active device. The simplest solution possible is a single gate, or multiple gate solution (for multiple outputs) that has a low threshold. The "T" version devices are fully specified to operate at 3.0 V. At this Voltage, they are low threshold. Table 1 shows the V_{IH} , V_{IL} for standard and "T" devices. V_{IH} , V_{IL} represent the requirements for a logic low and logic high. A CMOS device, lightly loaded will generally pull up/down to within 5% of V_{CC} and ground. A DSP/MCU operating at 1.7 V will pull up to 1.5 V, and down to 0.2 V (at 100 μ A). ON Semiconductor has many devices in the VHCT/LVXT family, such as MC74VHC1GT66, NLAST4501, NLAST4599, MC74LVXT4051, etc., that can be controlled without the need of translators.

Table 1. VHC/VHCT Device Comparison

Parameter	VHC	VHCT	V_{CC}
V_{IL}	1.5	0.8	5.0
V_{IH}	3.5	2.0	5.0
V_{IL}	0.9	0.53	3.0
V_{IH}	2.1	1.4	3.0

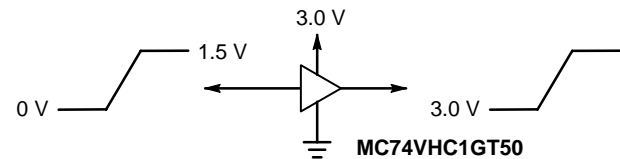


Figure 1. 1.5 V to 3.0 V Translator

CMOS logic becomes extremely slow below 2 V. Most families are not characterized below 2 V. We have come up with a simple solution to translate any 3–5 V input safely and with small delay. The only extra component is a single resistor. The device specified, is in the LCX family and is tolerant to voltages in excess of V_{CC} . The resistor can be as low as 100 Ω . The tradeoff is current and speed. A 100 Ω value would draw as high as 12 mA. Higher value resistors, would draw less current, but would add delay to the circuit. A 100 Ω resistor would add only 0.5 ns. As with the other illustrations, the Open Drain is available as a single gate (MC74VHC1G07) and hex version (MC74LCX07). The

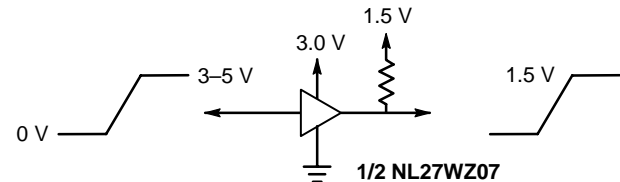



Figure 2. 3 V to 5 V Translator

device shown has a propagation delay of < 4.0 ns operating at 3.0 V, and a 1 K Ω pull-up would exhibit ≈ 5 ns delay with a light (5–10 pf) load. Inverting and non-inverting versions are also available, as well as open drain logic, in the MiniGate™ Logic family.

Conclusions: Logic level translation from extremely low voltages can be quite easy. ON Semiconductor offers,

inverting/non-inverting buffers, gates and analog switches in single, dual, triple (2H2001), hex, and octal. Open Drain devices in the VHC and LCX families will allow interface from higher voltages (as high as 5.5V) down to any voltage desired. These are also available in single, dual, triple (2H2001) and hex.

ON Semiconductor and  are trademarks of Semiconductor Components Industries, LLC (SCILLC). SCILLC reserves the right to make changes without further notice to any products herein. SCILLC makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does SCILLC assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation special, consequential or incidental damages. "Typical" parameters which may be provided in SCILLC data sheets and/or specifications can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals" must be validated for each customer application by customer's technical experts. SCILLC does not convey any license under its patent rights nor the rights of others. SCILLC products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the SCILLC product could create a situation where personal injury or death may occur. Should Buyer purchase or use SCILLC products for any such unintended or unauthorized application, Buyer shall indemnify and hold SCILLC and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that SCILLC was negligent regarding the design or manufacture of the part. SCILLC is an Equal Opportunity/Affirmative Action Employer.

PUBLICATION ORDERING INFORMATION

Literature Fulfillment:

Literature Distribution Center for ON Semiconductor
P.O. Box 5163, Denver, Colorado 80217 USA
Phone: 303-675-2175 or 800-344-3860 Toll Free USA/Canada
Fax: 303-675-2176 or 800-344-3867 Toll Free USA/Canada
Email: ONlit@hibbertco.com

N. American Technical Support: 800-282-9855 Toll Free USA/Canada

JAPAN: ON Semiconductor, Japan Customer Focus Center
4-32-1 Nishi-Gotanda, Shinagawa-ku, Tokyo, Japan 141-0031
Phone: 81-3-5740-2700
Email: r14525@onsemi.com

ON Semiconductor Website: <http://onsemi.com>

For additional information, please contact your local Sales Representative.