



---

## Design Example Report

<b>Title</b>	<b>2.4W Charger using TNY264P</b>
<b>Specification</b>	Input: 90 - 265 VAC Output: 6V / 0.4A
<b>Application</b>	Cell Phone Charger
<b>Author</b>	Power Integrations Applications Department
<b>Document Number</b>	DER-4
<b>Date</b>	February 4, 2004
<b>Revision</b>	1.0

### Summary and Features

This report details the design of an isolated Flyback converter for a wall mount adapter.

- Uses TinySwitch TNY264P
- Universal input voltage
- Typical Efficiency 62 % at 400 mA load
- Meets EN55022 Class B EMI tests with No Y capacitor
- Very low earth leakage current
- Meets tight CC over temperature with no thermistor

The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at [www.powerint.com](http://www.powerint.com)

## Table Of Contents

1	Introduction.....	5
2	Power Supply Specification.....	5
3	Schematic.....	6
4	PCB Layout.....	7
5	Bill Of Materials.....	8
6	Transformer.....	9
6.1	Transformer Winding.....	9
6.2	Electrical Specifications.....	9
6.3	Materials.....	9
6.4	Transformer Construction.....	10
6.5	Winding Instructions.....	11
6.6	Design Notes:.....	11
7	Performance Data.....	12
7.1	Efficiency.....	12
7.2	Regulation.....	13
7.3	No Load Input Power.....	13
7.4	Output Ripple Measurements.....	14
7.4.1	Ripple Measurement Technique.....	14
7.4.2	Output Voltage Ripple.....	15
8	EMI Tests.....	16
9	Revision History.....	18



## List Of Figures

Figure 1 – Flyback Converter – 2.4W 6V 0.4A.....	6
Figure 2 – PCB Layout .....	7
Figure 3 – Transformer Winding.....	9
Figure 4 – Transformer construction .....	10
Figure 5 – Efficiency Vs Output Current.....	12
Figure 6 – Load Regulation .....	13
Figure 7 – No Load Input Power.....	13
Figure 8 – Oscilloscope Probe Prepared for Ripple Measurement.....	14
Figure 9 – Oscilloscope Probe with Probe Master 5125BA BNC Adapter.....	14
Figure 10 – Output Voltage Ripple (worst case) at $V_{in} = 264 \text{ Vac}$ , $V_o = 6.0 \text{ V}$ , $I_o = 400 \text{ mA}$ .....	15
Figure 11 – EN55022 Class B, 110 Vac, Line (worst case), artificial hand connected to output return .....	16
Figure 12 – EN55022 Class B, 220 Vac, Line (worst case), artificial hand connected to output return .....	16
Figure 13 – EN55022 Class B, 110 Vac, Line (worst case), no artificial hand connected to output return ..	17
Figure 14 – EN55022 Class B, 220 Vac, Line (worst case), no artificial hand connected to output return ..	17

## List Of Tables

Table 1 – Power Supply Specification .....	5
Table 2 – Bill of Materials.....	8
Table 3 – Transformer BOM.....	9

### Important Notes:

Although this board is designed to satisfy safety isolation requirements, the engineering prototype has not been agency approved. Therefore, all testing should be performed using an isolation transformer to provide the AC input to the prototype board.

Design Reports contain a power supply design specification, schematic, bill of materials, and transformer documentation. Performance data and typical operation characteristics are included. Typically only a single prototype has been built.





## 1 Introduction

This document is an engineering report giving performance characteristics of an isolated Flyback converter with universal input voltage and 6V 0.4A output CV / CC characteristics. This design uses TinySwitch – an integrated IC comprising a high voltage MOSFET, PWM controller.

This document contains the power supply specification, schematic, and bill of materials, transformer documentation, printed circuit layout, and performance data.

## 2 Power Supply Specification

Description	Symbol	Min	Typ	Max	Units	Comment
<b>Input</b> Voltage	$V_{IN}$	90		265	Vac	
<b>Output</b> Output Voltage	$V_{OUT1}$	5.7	6.0	6.3	V	in constant voltage mode
Output Ripple Voltage 1	$V_{RIPPLE1}$			150	mV	20 MHz Bandwidth
Output Current	$I_{OUT1}$	375		425	mA	in constant current mode
<b>Total Output Power</b> Continuous Output Power	$P_{OUT}$			2.4	W	
<b>Conducted EMI Margin</b>		5			dB	EN550022 B, FCC B
<b>Efficiency</b>	$\eta$		50		%	At full load
Ambient Temperature	$T_{AMB}$	-10		40	°C	Free convection, Sea level

Table 1 – Power Supply Specification





### 4 PCB Layout

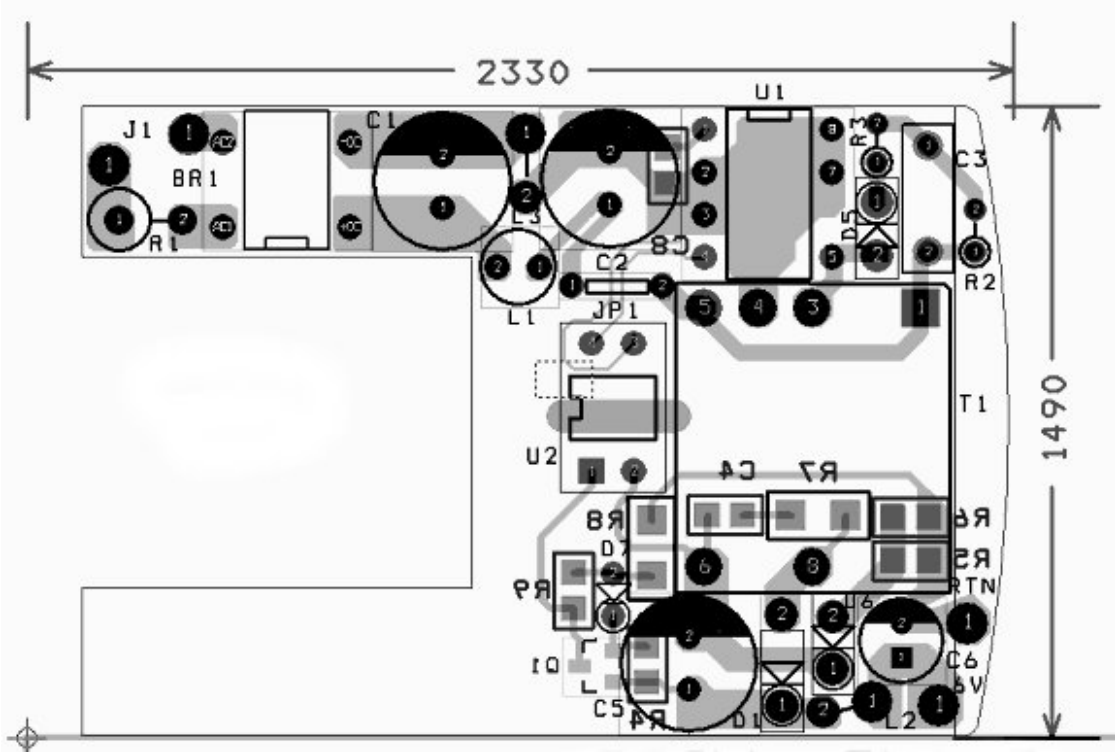


Figure 2 – PCB Layout



## 5 Bill Of Materials

Item	Qty	Reference	Part
1	1	BR1	DF06, 600 V, 1A, bridge rectifier
2	2	C1, C2	4.7 $\mu$ F, 400V, AL electrolytic capacitor
3	1	C3	4700 pF, 1KV, ceramic capacitor
4	1	C4	1000 pF, 100V, 0805, ceramic capacitor
5	1	C5	470 $\mu$ F, 10V, AL electrolytic low ESR capacitor
6	1	C6	100 $\mu$ F, 10V, AL electrolytic low ESR capacitor
7	1	C8	0.1 $\mu$ F, 50V, 0805, ceramic capacitor
8	1	D1	UG1B, 100V, 1A, 15 nSec, UFR
9	1	D5	1N4007GP, 1000V, 1A, 2 $\mu$ S, glass passivated diode
10	1	D6	1N4001, 50V, 1A, diode
11	1	D7	BZX79C5.6V, zener, 5.6V, 0.5W, 2%
12	1	JP1	Jumper wire, # 22 AWG, 0.5 "
13	1	L1	1 mH Inductor
14	1	L2	Large Ferrite Bead
15	1	L3	1mH or Large ferrite bead ( <i>optional</i> )
16	1	Q1	MMBT3906, PNP transistor, 40V, 200 mA
17	1	R1	10 $\Omega$ , 1W, fusible resistor
18	1	R2	200 K $\Omega$ , 1/8W, 5%
19	1	R3	240 $\Omega$ , 1/8W, 5%
20	1	R4	330 $\Omega$ , 0805, 5%,
21	2	R5, R6	1.1 $\Omega$ , 0805, 1%,
22	1	R7	5.1 $\Omega$ , 1206, 5%
23	1	R8	0 $\Omega$ , 1206, 5%,
24	1	R9	100 $\Omega$ , 0805, 1%
25	1	R10	10 K $\Omega$ , 1206, 5%, ( <i>optional</i> )
26	1	T1	Flyback Transformer
27	1	U1	TNY264P
28	1	U2	PC817D, Optocoupler, CTR = 300 - 600 %

Table 2 – Bill of Materials





## 6 Transformer

### 6.1 Transformer Winding

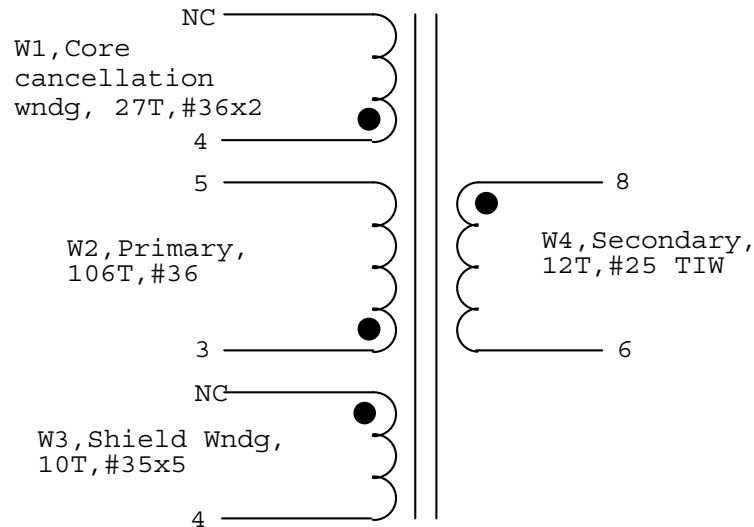


Figure 3 – Transformer Winding

### 6.2 Electrical Specifications

Electrical Strength	60Hz 1minute, from Pins 3-5 to Pins 6-8	3 kV for 1 minute
Primary Inductance (Pin 3 to Pin 5)	All windings open	1.78 mH – 2.05 mH
Resonant Frequency	All windings open	300 kHz min.
Primary Leakage Inductance	L <sub>35</sub> with pins 6-8 shorted	60 μH max.

### 6.3 Materials

Item	Description
[1]	Core: EE16, TDK Gapped for $A_L = 158.5 \text{ nH/T}^2 - 182.4 \text{ nH/T}^2$
[2]	Bobbin: Horizontal 10 pins
[3]	Magnet Wire: #35 AWG
[4]	Magnet Wire: #36 AWG
[5]	Triple Insulated wire: # 25 AWG
[6]	Tape: 3M 1298 Polyester Film (white) 0.311" x 2 mils
[7]	Varnish

Table 3 – Transformer BOM

### 6.4 Transformer Construction

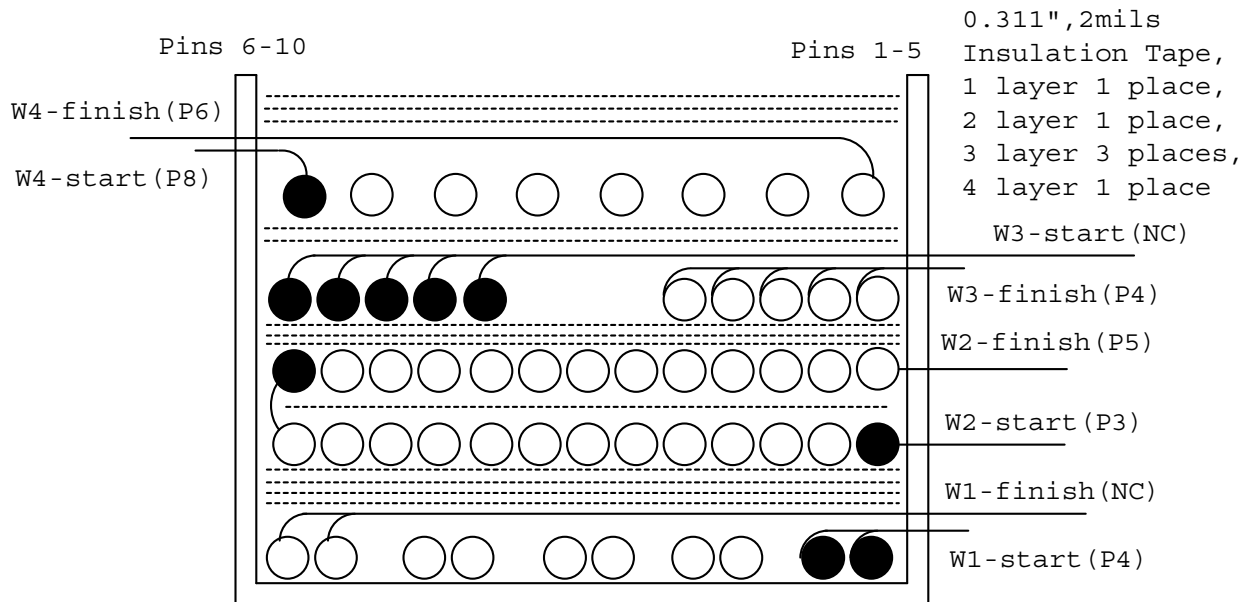


Figure 4 – Transformer construction

### 6.5 Winding Instructions

Place the bobbin on the winding machine with pins 1-5 on the right side and pins 6-10 on the left side.

W1 (Shield/ core cancellation winding)	Wind 27 turns from right to left with # 36 x 2 (bifilar) AWG magnet wire starting from pin 4 and leave the finishing end open, bend the finishing end 90° and cut the wire in the middle of the bobbin width.
Basic Insulation	4 layers of tape for insulation.
W2 (Primary Winding)	Wind 106 turns in 2 layers with # 36 AWG magnet wire – first layer 53T from right to left starting from pin 3 – one layer of insulation tape – second layer 53T from left to right and finishing at pin 5.
Basic Insulation	3 layers of tape for insulation.
W3 (Shield winding)	Wind 10 turns with #35 x 5 (penta-filar) magnet wire from left to right starting temporarily from pin 8, and finishing at pin 4. Extend the start end to cover any gap, then bend 90° and cut the wire in the middle of the bobbin width.
Basic Insulation	2 layers of tape for insulation.
W4 (Secondary Winding)	Wind 12 turns with # 25 triple insulated wire from left to right starting from 8 and finishing at 6.
Outer Insulation	3 layers of tape for insulation.
Core Assembly	Assemble and secure core halves.
Final Assembly	Impregnate transformer uniformly with varnish.

### 6.6 Design Notes:

Power Integrations Device	TNY264P
Frequency of Operation	132 KHz
Mode	Continuous/ discontinuous
Peak Current	0.25 A
Reflected Voltage (Secondary to Primary)	71.5 V
Maximum AC Input Voltage	264 V
Minimum AC Input Voltage	90 V



## 7 Performance Data

All measurements are performed at room temperature unless otherwise specified. The output voltages are measured at the end of a 6-foot cable with 0.2 Ω total resistance.

### 7.1 Efficiency

The measurements are made for various load and line conditions. The efficiencies are calculated and shown in Figure 5.

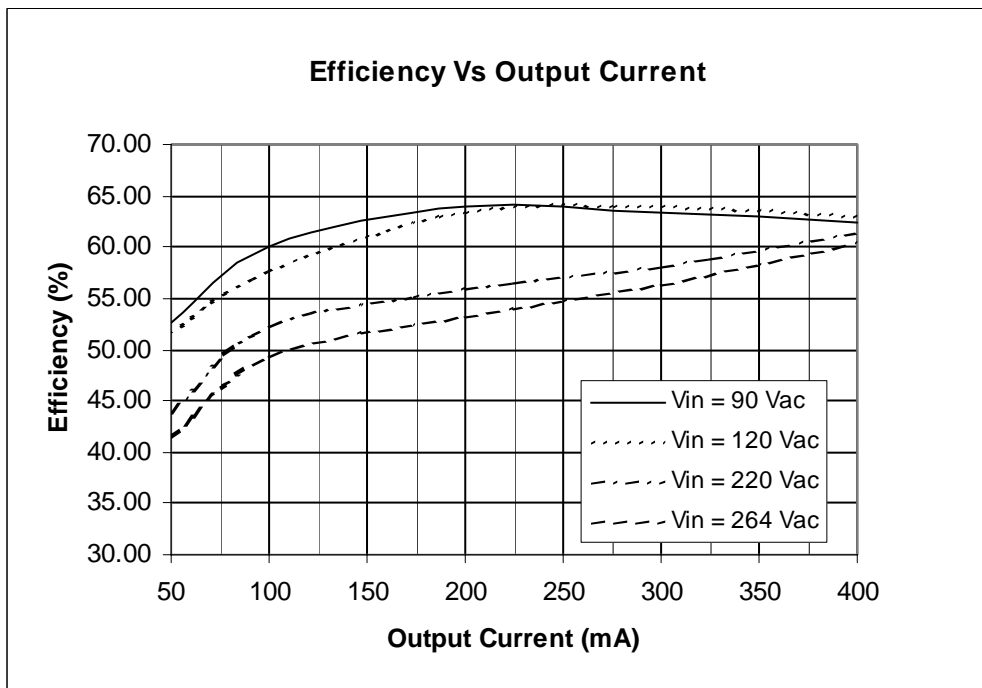


Figure 5 – Efficiency Vs Output Current



**7.2 Regulation**

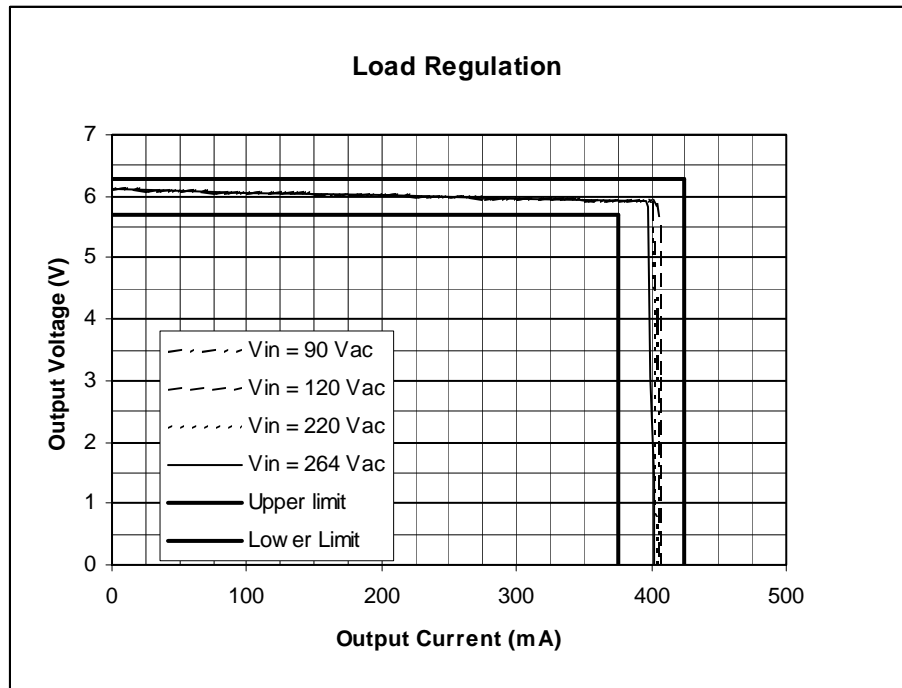


Figure 6 – Load Regulation

**7.3 No Load Input Power**

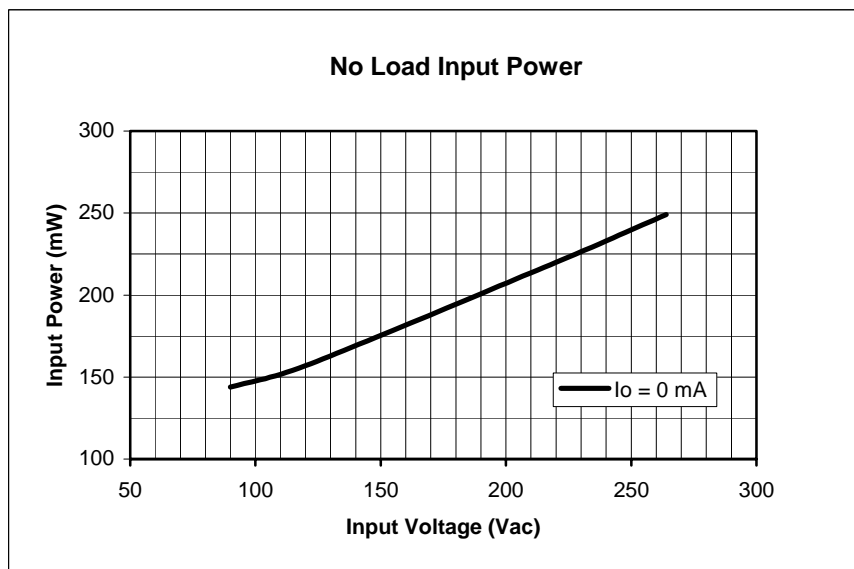


Figure 7 – No Load Input Power




## 7.4 Output Ripple Measurements


### 7.4.1 Ripple Measurement Technique

For DC output ripple measurements, a modified oscilloscope test probe must be utilized in order to reduce spurious signals due to pickup. Details of the probe modification are provided in Figure 8 and Figure 9.

The 5125BA probe adapter is affixed with two capacitors tied in parallel across the probe tip. The capacitors include one (1) 0.1  $\mu\text{F}/50\text{ V}$  ceramic type and one (1) 1.0  $\mu\text{F}/50\text{ V}$  aluminum electrolytic. *The aluminum electrolytic type capacitor is polarized, so proper polarity across DC outputs must be maintained (see below).*

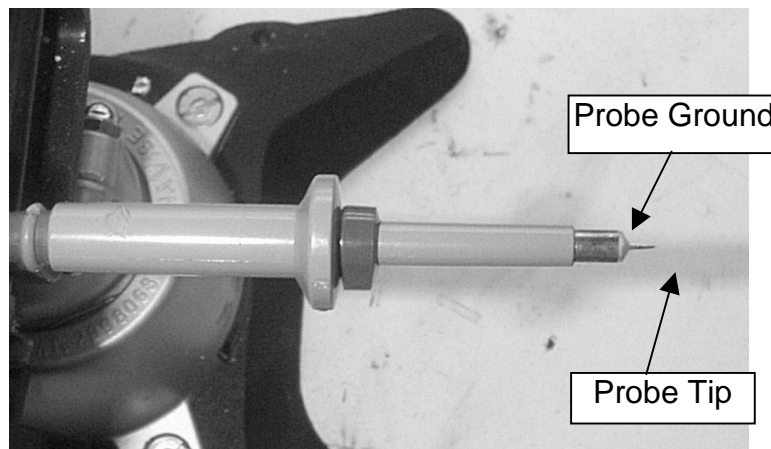

**Figure 8** – Oscilloscope Probe Prepared for Ripple Measurement.  
(End Cap and Ground Lead Removed)

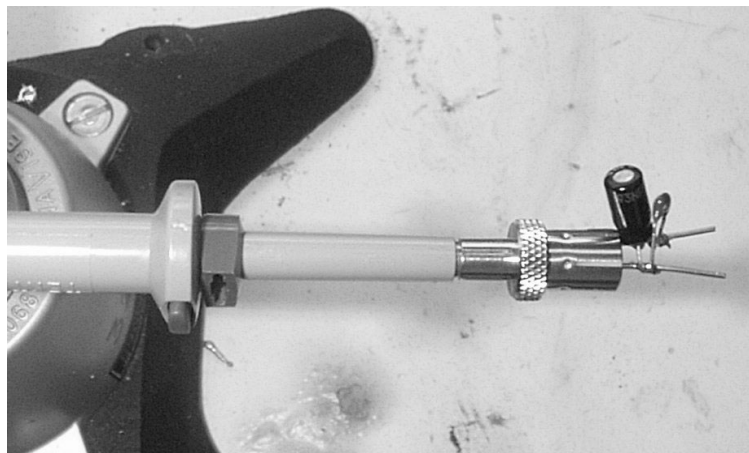

**Figure 9** – Oscilloscope Probe with Probe Master 5125BA BNC Adapter

(Modified with wires for probe ground for ripple measurement, and two parallel decoupling capacitors added).

## 7.4.2 Output Voltage Ripple

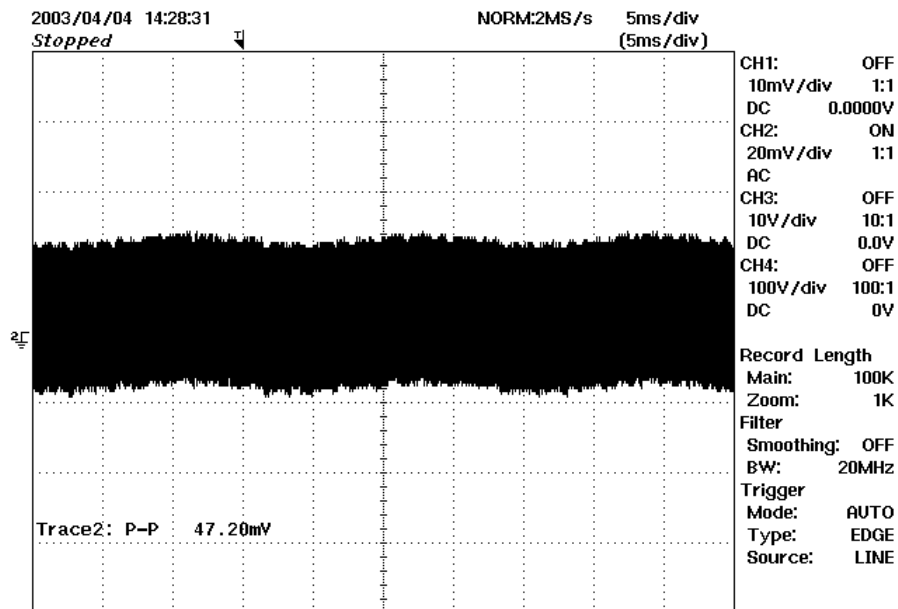


Figure 10 – Output Voltage Ripple (worst case) at  $V_{in} = 264$  Vac,  $V_o = 6.0$  V,  $I_o = 400$  mA



### 8 EMI Tests

The EMI tests are done at 110 Vac and 220 Vac inputs, Line (worst case) and 15 Ω (395 mA approx.) load. To obtain more margin in radiated EMI, use *L3 = Long ferrite bead*. With *L3 = 1 mH* and *R10 = 5.1 KΩ*, radiated EMI will improve even more, and conducted EMI will also improve.

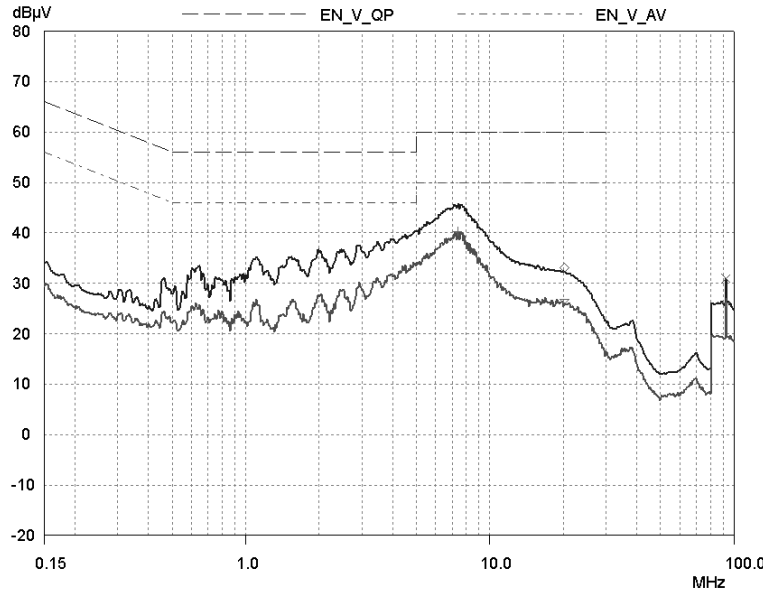


Figure 11 – EN55022 Class B, 110 Vac, Line (worst case), artificial hand connected to output return

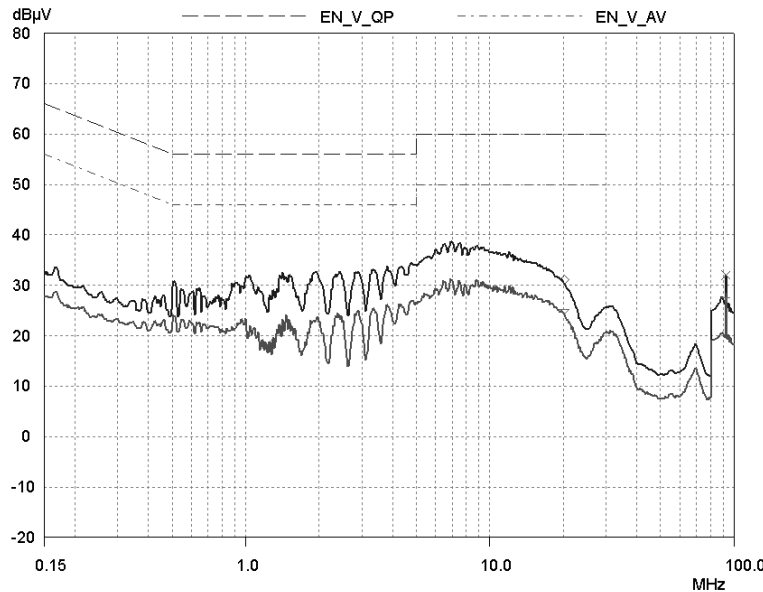


Figure 12 – EN55022 Class B, 220 Vac, Line (worst case), artificial hand connected to output return





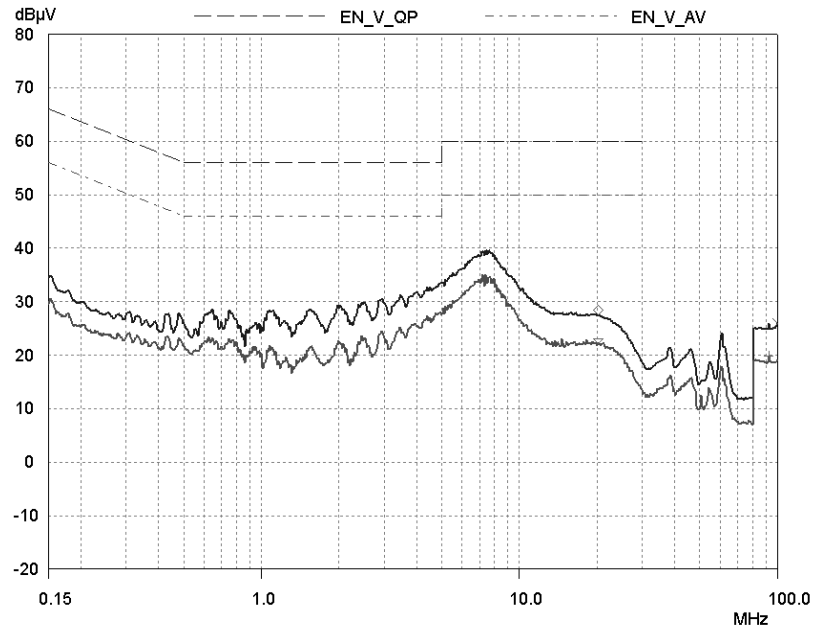


Figure 13 – EN55022 Class B, 110 Vac, Line (worst case), no artificial hand connected to output return

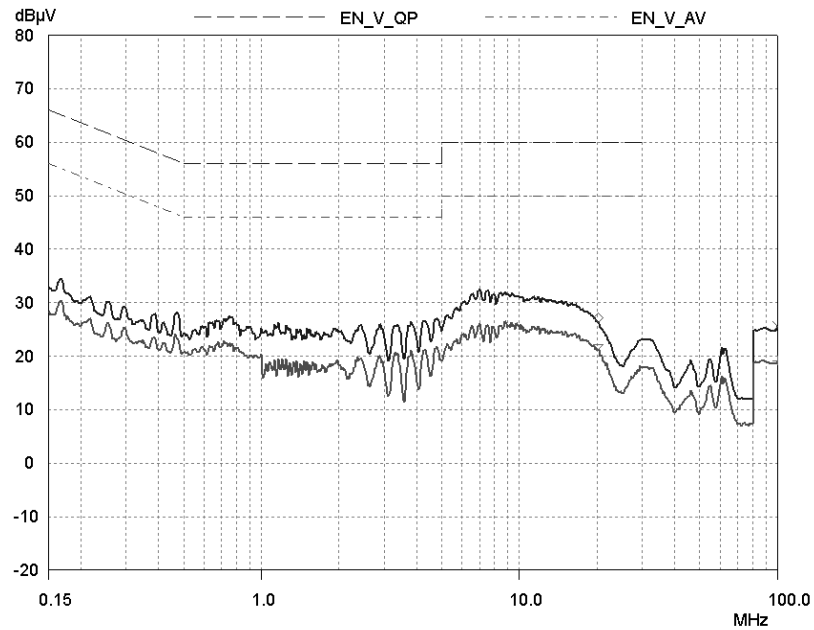


Figure 14 – EN55022 Class B, 220 Vac, Line (worst case), no artificial hand connected to output return



## 9 Revision History

<b>Date</b>	<b>Author</b>	<b>Revision</b>	<b>Description &amp; changes</b>	<b>Reviewed</b>
February 4, 2004	MJ	1.0	First Release	AM/VC



**Notes**



For the latest updates, visit our Web site: [www.powerint.com](http://www.powerint.com)

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others.

The products and applications illustrated herein (including circuits external to the products and transformer construction) may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at [www.powerint.com](http://www.powerint.com).

The PI Logo, **TOPSwitch**, **TinySwitch**, **LinkSwitch**, and **EcoSmart** are registered trademarks of Power Integrations, Inc. **PI Expert** and **DPA-Switch** are trademarks of Power Integrations, Inc.  
© Copyright 2003, Power Integrations, Inc.

**WORLD HEADQUARTERS  
NORTH AMERICA - WEST**  
Power Integrations  
5245 Hellyer Avenue  
San Jose, CA 95138 USA.  
Main: +1•408•414•9200  
Customer Service:  
Phone: +1•408•414•9665  
Fax: +1•408•414•9765

**NORTH AMERICA - EAST  
& SOUTH AMERICA**  
Power Integrations, Inc.  
Eastern Area Sales Office  
1343 Canton Road, Suite C1  
Marietta, GA 30066 USA  
Phone: +1•770•424•5152  
Fax: +1•770•424•6567

**EUROPE & AFRICA**  
Power Integrations (Europe) Ltd.  
Centennial Court  
Easthampstead Road  
Bracknell  
Berkshire RG12 1YQ,  
United Kingdom  
Phone: +44•1344•462•301  
Fax: +44•1344•311•732

**TAIWAN**  
Power Integrations International  
Holdings, Inc.  
2F, #508, Chung Hsiao E. Rd.,  
Sec. 5,  
Taipei 105, Taiwan  
Phone: +886•2•2727•1221  
Fax: +886•2•2727•1223

**CHINA**  
Power Integrations  
International  
Holdings, Inc.  
Rm# 1705, Bao Hua Bldg.  
1016 Hua Qiang Bei Lu  
Shenzhen Guangdong,  
518031  
Phone: +86•755•367•5143  
Fax: +86•755•377•9610

**KOREA**  
Power Integrations  
International  
Holdings, Inc.  
Rm# 402, Handuk Building,  
649-4 Yeoksam-Dong,  
Kangnam-Gu,  
Seoul, Korea  
Phone: +82•2•568•7520  
Fax: +82•2•568•7474

**JAPAN**  
Power Integrations, K.K.  
Keihin-Tatemono 1st Bldg.  
12-20 Shin-Yokohama 2-  
Chome,  
Kohoku-ku, Yokohama-shi,  
Kanagawa 222, Japan  
Phone: +81•45•471•1021  
Fax: +81•45•471•3717

**INDIA (Technical Support)**  
Innovatech  
#1, 8th Main Road  
Vasanthnagar  
Bangalore, India 560052  
Phone: +91•80•226•6023  
Fax: +91•80•228•9727

**APPLICATIONS HOTLINE**  
World Wide +1•408•414•9660

**APPLICATIONS FAX**  
World Wide +1•408•414•9760

