

# Design Idea DI-27

## TinySwitch® 3 W AC Adapter: <10 mW No-load Consumption



Application	Device	Power Output	Input Voltage	Output Voltage	Topology
Adapter	TNY254	3 W	85-265 VAC	12 V	Flyback

### Design Highlights

- Extremely low no-load power consumption (<10 mW at 115/230 VAC input)
- Simple RC snubber/clamp reduces EMI
- Low cost, low component count solution

### Operation

The *TinySwitch* flyback converter in Figure 1 generates an isolated 12 VDC, 3 W output from 85 VAC to 265 VAC input. Typical applications include wall mounted AC adapters for consumer products.

The key performance characteristic of the circuit shown is extremely low no-load consumption of <10 mW. A linear transformer adapter of similar rating will typically consume 1 W to 4 W at no-load. At \$0.12/kWh, the *TinySwitch* can therefore reduce energy costs by \$1 to \$4 per year.

The no-load performance is achieved using a transformer bias winding as a low voltage source for *TinySwitch* operating current. Even without this winding, a *TinySwitch* circuit will

consume <100 mW at no-load. However, by providing external bias, the internal high voltage current source, which normally powers the IC from the DRAIN pin, is disabled and a further reduction in consumption is therefore achieved.

The bias winding should provide enough current to fully disable the internal current source. Figure 2 shows that the bias winding and choice of C5 and R3 should provide 250  $\mu$ A to 300  $\mu$ A at no-load to minimize consumption. Zener VR3 is required to clamp the BYPASS pin voltage.

The output Zener VR2 is not biased, minimizing the secondary circuit consumption. A low current Zener therefore provides the best output voltage tolerance.

Components R2 and C3 provide a low cost clamp and also help reduce EMI by softening switching edges. This type of snubber increases switching losses and would therefore normally be avoided in low consumption circuits. However, with *TinySwitch*, these losses are negligible at no-load as switching frequency is so low. This is illustrated in Figure 3 where replacing R2 and C3 with a Zener clamp across the primary winding reduces consumption by <0.25 mW.

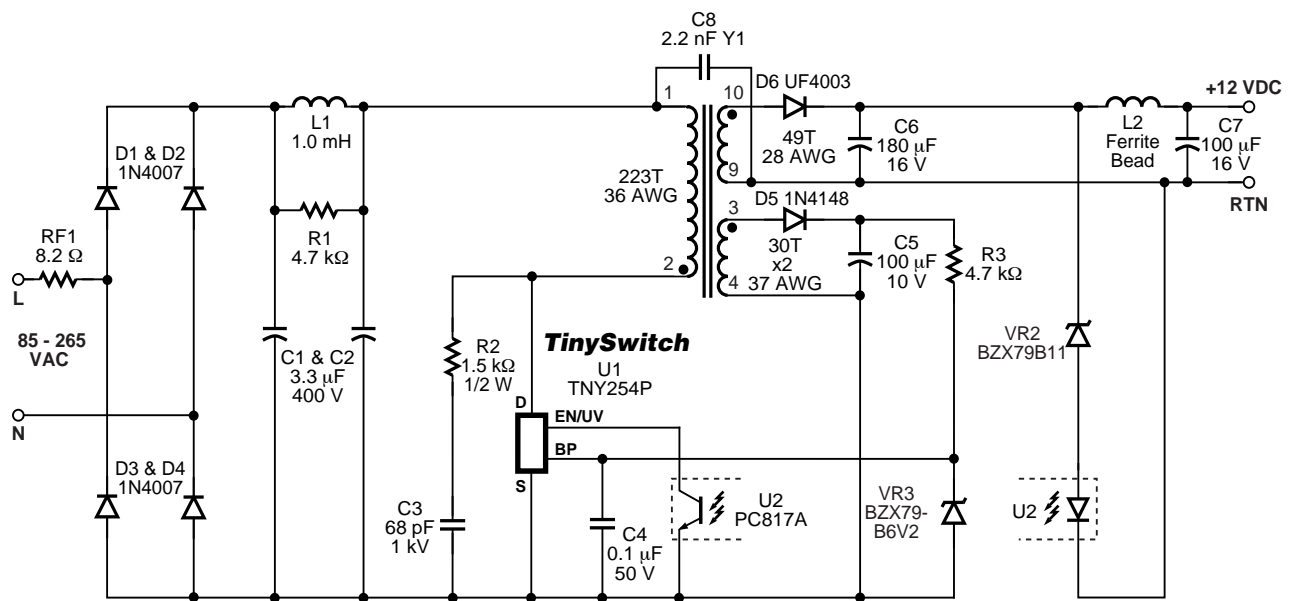


Figure 1. 3 W AC Adapter with <10 mW No-load Consumption.

PI-3011-091802

## Key Design Points

- Design bias winding circuit to provide 250  $\mu\text{A}$  to 300  $\mu\text{A}$  at no-load.
- Ensure C5 is large enough to supply above current at the very low no-load switching frequencies.
- Minimize secondary circuit bias currents. Use low current feedback Zeners for best tolerance.
- Zener or RCD clamp can be used to slightly reduce no-load consumption further. Use a 200 V Zener or maximize resistor value in RCD clamp for lowest losses.
- Design transformer with low reflected voltage to minimize clamp losses.
- Wind transformer for lowest leakage inductance. Choose wire gauges to completely fill winding layers.
- Wind transformer with tape between primary layers to further reduce intra-winding capacitance.

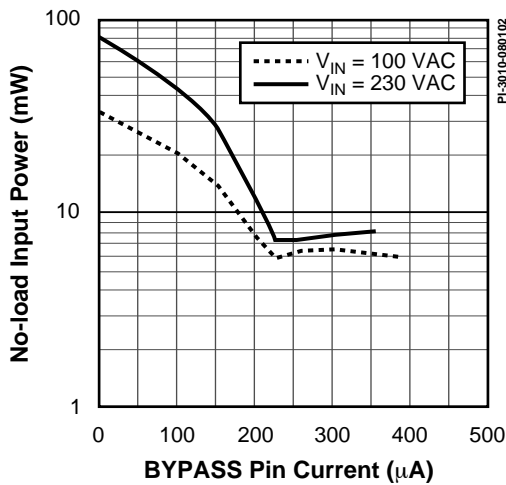


Figure 2. No-load Input Power vs. BYPASS Pin Current.

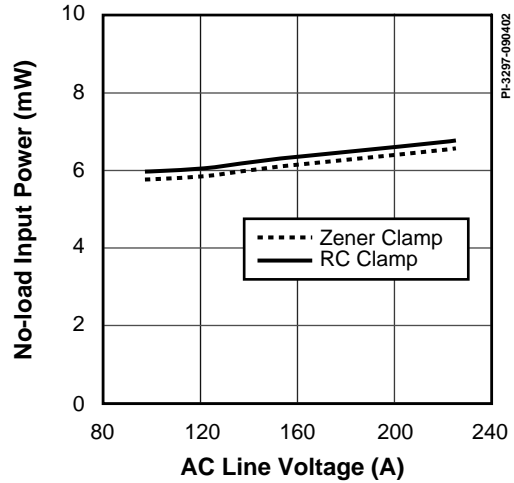


Figure 3. No-load Input Power Variation with Input Voltage.

TRANSFORMER PARAMETERS	
Core Material	EE16 Nippon Ceramic NC-2H $A_L$ of 74 nH/T <sup>2</sup>
Bobbin	EE16 10 pin (Ying Chin YC1607 or equivalent)
Winding Order (pin numbers)	Primary (1-2), Tape 12 V (10-9), Tape Bias (3-4), Tape
Primary Inductance	3.67 mH $\pm$ 10%
Primary Resonant Frequency	500 kHz (minimum)
Leakage Inductance	300 $\mu\text{H}$ (maximum)

Table 1. Transformer Construction Information.

For the latest updates, visit our Web site: [www.powerint.com](http://www.powerint.com)

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein, nor does it convey any license under its patent rights or the rights of others. The products and applications illustrated herein may be covered by one or more U.S. and foreign patents or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at [www.powerint.com](http://www.powerint.com).

The PI Logo, **TOPSwitch**, **TinySwitch** and **EcoSmart** are registered trademarks of Power Integrations, Inc. **PI Expert** is a trademark of Power Integrations, Inc. ©Copyright 2002, Power Integrations, Inc.

### WORLD HEADQUARTERS AMERICAS

Power Integrations, Inc.  
San Jose, CA 95138 USA  
Customer Service:  
Phone: +1 408-414-9665  
Fax: +1 408-414-9765  
e-mail: [usasales@powerint.com](mailto:usasales@powerint.com)

### CHINA

Power Integrations International  
Holdings, Inc.  
China  
Phone: +86-755-8367-5143  
Fax: +86-755-8377-9610  
e-mail: [chinasales@powerint.com](mailto:chinasales@powerint.com)

### EUROPE & AFRICA

Power Integrations (Europe) Ltd.  
United Kingdom  
Phone: +44-1344-462-300  
Fax: +44-1344-311-732  
e-mail: [eurosales@powerint.com](mailto:eurosales@powerint.com)

### KOREA

Power Integrations  
International Holdings, Inc.  
Seoul, Korea  
Phone: +82-2-782-2840  
Fax: +82-2-782-4427  
e-mail: [koreasales@powerint.com](mailto:koreasales@powerint.com)

### SINGAPORE

Power Integrations, Singapore  
Republic of Singapore 308900  
Phone: +65-6358-2160  
Fax: +65-6358-2015  
e-mail: [singaporesales@powerint.com](mailto:singaporesales@powerint.com)

### JAPAN

Power Integrations, K.K.  
Keihin-Tatemono 1st Bldg.  
Japan  
Phone: +81-45-471-1021  
Fax: +81-45-471-3717  
e-mail: [japansales@powerint.com](mailto:japansales@powerint.com)

### APPLICATIONS HOTLINE

World Wide +1-408-414-9660

### TAIWAN

Power Integrations  
International Holdings, Inc.  
Taipei, Taiwan  
Phone: +886-2-2727-1221  
Fax: +886-2-2727-1223  
e-mail: [taiwansales@powerint.com](mailto:taiwansales@powerint.com)

### INDIA (Technical Support)

Innovatech  
Bangalore, India  
Phone: +91-80-226-6023  
Fax: +91-80-228-9727  
e-mail: [indiasales@powerint.com](mailto:indiasales@powerint.com)

### APPLICATIONS FAX

World Wide +1-408-414-9760

