

Applying the DLX3416* Intelligent Display[®] Device Appnote 17

This application note is intended to serve as a design and application guide for users of the DLX3416 (referred to as 3416 hereafter) alphanumeric Intelligent Displays. This appnote also covers device electrical description and operation, considerations for general circuit design, and interfacing the 3416 to microprocessors. Refer to the specific data sheet and other Infineon / OSRAM Appnotes for more details.


Electrical & Mechanical Description

The internal electronics in these Intelligent Displays eliminates all the traditional difficulties of using multi-digit light emitting displays (segment decoding, drivers, and multiplexing).

An Intelligent Display also provides internal memory for four digits. This approach allows the user to asynchronously address one of four digits, and load new data without the LED multiplex timing.

Figure 1 is a block diagram of the DLX3416. The device consists of four (5x7) LED arrays and a single CMOS integrated circuit. The IC chip contains the column and row drivers, ROM, four word x7 bit Random Access Memory, multiplexing, multiplex counter/decoder, cursor address decoder, and miscellaneous control logic.

Figure 1. Block diagram—DLX3416

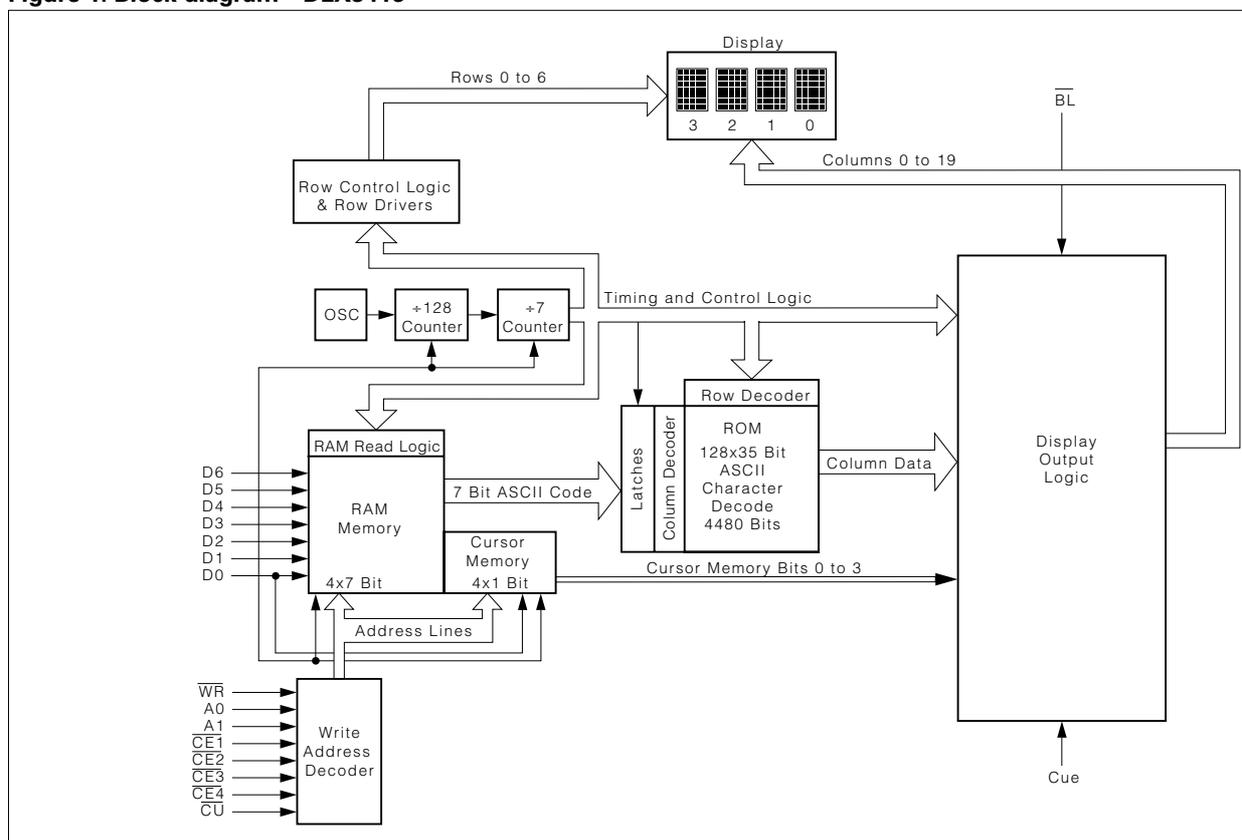

Packaging

Packaging consists of a transfer molded nylon lens which also serves as an “encapsulation shell” since it covers five of the six “faces.” The assembled and tested substrate (“PTF” multi-layer), is placed within the shell and the entire assembly is then filled with a water clear IC grade epoxy.

This yields a very rugged part, which is quite impervious to moisture, shock and vibration. Although not “hermetic,” the device will easily withstand total immersion in water/detergent solutions.

Figure 2. Top view

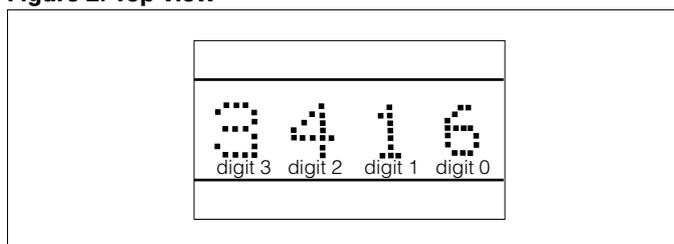


Table 1. Pin outs

Pin	Function	Pin	Function
1	$\overline{CE1}$ Chip Enable	10	GND
2	$\overline{CE2}$ Chip Enable	11	D0 Data Input
3	\overline{CLR} Clear	12	D1 Data Input
4	CUE Cursor Enable	13	D2 Data Input
5	\overline{CU} Cursor Select	14	D3 Data Input
6	\overline{WR} Write	15	D6 Data Input
7	A1 Digit Select	16	D5 Data Input
8	A0 Digit Select	17	D4 Data Input
9	V_{CC}	18	\overline{BL} Display Blank

Table 2. Electrical inputs to the 3416

V_{CC}	Positive supply +5 volts
GND	Ground
D0-D6	Data Lines The seven data input lines are designed to accept the first 64 ASCII characters. Figure 3 for DL3416 character set. The device interprets all undefined codes as blank. See Figure 3 for DLX3416 character set.
A0, A1	Address Lines The address determines the digit position which the data will be written. A0 is right to left for positive-true logic.
\overline{WR}	Write (Active Low) Data and address to be loaded must be present and stable before and after the edge of write. (See DL3416, DLX3416 sheets for timing information).
$\overline{CE1}, \overline{CE2}$	Chip Enable (Active High)
$\overline{CE3}, \overline{CE4}$	Chip Enable (Active Low) Determines which device in an array accept data. When either or both chip enable is in the high state, the device are inhibited.
\overline{CLR}	Clear (Active Low) The data RAM and cursor RAM of the DL3416 will be cleared when held low. The minimum for the \overline{CLR} is 1 ms. (See DLX3416).
CUE	Cursor Enable Activates Cursor function. Cursor is displayed regardless of cursor memory contents when cue is Low.
\overline{CU}	Cursor Select (Active Low) This input must be held high to store data memory and low to store cursor memory.
\overline{BL}	Display Blank (Active Low) Blanking the entire display may be accomplished by holding the \overline{BL} input low. When \overline{BL} is released, the stored function. When \overline{BL} is released, the stored characters are again displayed. \overline{BL} may be used for flashing or dimming.

Figure 3. Character set—DLX3416

ASCII CODE		D0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	
D6	D5	D4	HEX	0	1	2	3	4	5	6	7	8	9	A	B	C	D	E	F
0	0	0	0	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·
0	0	1	1	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·
0	1	0	2	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·
0	1	1	3	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·
1	0	0	4	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·
1	0	1	5	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·
1	1	0	6	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·
1	1	1	7	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·	·

Notes: 1. High = 1 level.
 2. Low = 0 level.
 3. Upon power up, the device will initialize in a random state.

Clear Memory

Clearing of the entire internal four digit memory may be accomplished by holding the clear line (CLR) low for one complete internal display multiplex cycle, 15 mS minimum for DL 3416, 1 mS for DLX3416. Less time may leave some data uncleared. CLR also clears the cursor memory.

Display Blanking


Blanking the display may be accomplished by loading a blank, space or illegal code into each digit of the display or by using the (BL) display blank input. Setting the (BL) input low does not affect the contents of either data or cursor memory. A flashing display can be realized by pulsing (BL).

Operation

Multiplexed display systems sequentially read and display data from a memory device. In synchronous systems, control circuitry must compare the location of data to be read to the location or position of new data to be stored or displayed, i.e., synchronize before a Write can be done. This can be slow and cumbersome.

Data entry in Intelligent Displays is asynchronous and may be done in any random order. Loading data is similar to writing into a RAM. Each digit has its own memory location and will display until replaced by another code.

Figure 4. Write cycle waveforms

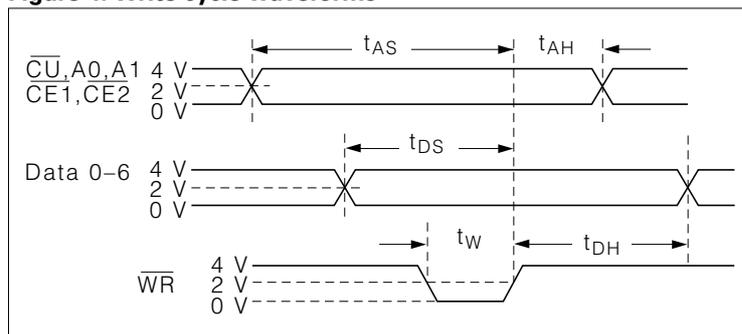

The waveforms of Figure 4 demonstrate the signal relationships of the signals required to generate a write cycle. (Check individual data sheet for minimum pulse widths.) From the waveforms, all signals are seen to be active low, and all signals are sampled from the rising or trailing edge of write.

Cursor

The DLX3416 cursor function causes all digits to be displayed at 50% brightness. The cursor can be used to indicate the position in the display of the next character to be entered. The cursor is not a character but a position in the display of a stored character. Upon writing a character to the cursor, the display will again show the character stored in memory.

The cursor can be written into any digit position by setting the cursor enable (CUE) high, setting the cursor address (A1, A0), enabling Chip Enable, (CE1, CE2), cursor select (\overline{CU}), Write (\overline{WR}) and Data (D0-D6). Data line D0 will place a cursor into the position indicated by address A0 and A1. Conversely, a low on the cursor select (\overline{CU}) and write (\overline{WR}) signals have been used to clear the cursor. During the cursor-write sequence, data lines D6 are ignored by the 3416.

If the user does not wish to utilize the cursor function, the cursor enable (CUE) can be tied low to disable the cursor function. A flashing cursor can be realized by simply pulsing the CUE line after cursor data has been stored.

General Design Considerations

Using Positive true logic, address order is left to right. For left to right address order, use the "complement" or simple inversion of the address lines.

For systems with only a 6 bit (abbreviated) address format, Data Line D6 cannot be left open. It should be the complement of Data Line D5.

A "display test" or "lamp test" function can be realized by simply storing a cursor into all digits.

Because of the random state of the cursor memories at power up, if the cursor function is to be used, it is necessary to clear cursors initially to assure that all cursor memories contain its zero state. This can be accomplished with the CLR input.

When using the 3416 on a separate display board with more than 6 inches of cable length, it may be necessary to buffer all inputs. This is most easily accomplished with non-inverting buffers such as the 74365. To prevent transient current in the protection diodes, the buffers should be located on the display board rather than the displays.

Local power supply bypass capacitors are recommended in many cases. These should be 6 or 10 volt electrolytic with 10 μ F or greater capacitance. Low inductance is important due to current steps which occur from the internal multiplexing of the display.

If small wire cables are used, it is good engineering practice to calculate the wire resistance of the cables. The +5 volt wires. More than 0.1 volt drop

digit worst cast) should be avoided, since this loss is in addition to any inaccuracies or load regulation limitations of the power supply.

The 5 volt power supply for the displays should be the same one supplying V_{CC} to all logic devices which drive the display devices. If a separate supply must be used, then local buffers using hex non-inverting gates should be used on all inputs and these buffers should be powered from the display power supply. This precaution is to avoid logic inputs higher than display V_{CC} during power up or line transients.

Figure 5.

Loading Data

BL	CE1	CE2	CUE	CU	WR	CLR	A ₁	A ₀	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Digit 3	Digit 2	Digit 1	Digit 0
L	X	X	X	H	X	H	X	X	X	X	X	X	X	X	X				
H	H	X	L	H	X	H	X	X	X	X	X	X	X	X	X				
H	X	H	L	H	X	H	X	X	X	X	X	X	X	X	X				
H	X	X	L	H	H	H	X	X	X	X	X	X	X	X	X				
H	L	L	L	H	L	H	L	L	H	L	L	L	L	L	H				
H	L	L	L	H	L	H	L	H	H	L	L	L	L	L	H				
H	L	L	L	H	L	H	H	H	H	L	L	L	L	H	L				
H	L	L	L	H	L	H	H	H	H	L	L	L	L	H	L				
H	L	L	L	H	L	H	H	L	L	L	L	L	H	L	H				
H	L	L	L	H	L	H	H	L	L	L	L	H	L	H	H				
H	L	L	L	H	L	H	-	-	-	-	-	-	-	-	-				

Loading Cursor


BL	CE1	CE2	CUE	CU	WR	CLR	A ₁	A ₀	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Digit 3	Digit 2	Digit 1	Digit 0
L	X	X	X	H	X	H	X	X	X	X	X	X	X	X	X				
H	L	L	L	H	H	H	H	X	X	X	X	X	X	X	X				
H	L	L	L	H	L	L	H	L	X	X	X	X	X	X	H				
H	L	L	L	H	L	L	H	L	H	X	X	X	X	X	H				
H	L	L	L	H	L	L	H	H	L	X	X	X	X	X	H				
H	L	L	L	H	L	L	H	H	X	X	X	X	X	X	H				
H	L	L	L	H	L	L	H	X	X	X	X	X	X	X	X				
H	L	L	L	H	L	L	H	L	L	X	X	X	X	X	L				
H	L	L	L	H	L	H	X	X	X	X	X	X	X	X	X				

X = Don't care
 NC = No change from previously displayed characters
 ■ = all dots/segments on at half brightness

Interfacing the 3416

A general and straightforward interface circuit is shown in Figure 6. This scheme can easily interface to μP systems or any other systems which can provide the seven data lines, appropriate address, and control lines.

Figure 6. General interface circuit

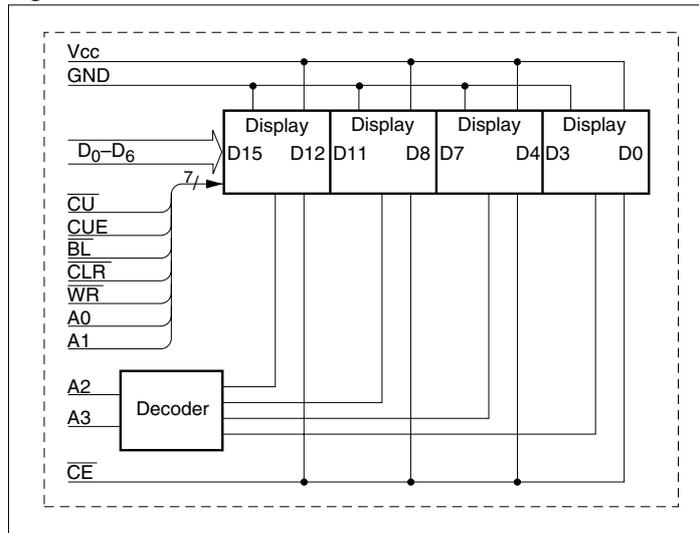

Parallel I/O

The parallel I/O device of a microprocessor can be connected to the circuit in Figure 6. One eight bit port can provide the seven input data bits and the cursor enable. Another eight bit output port can contain the cursor chip enable information and the other control lines.

INIT:	MVI A,80H OUT CONTROL	;CONTROL DATA ;LOAD CONTROL
CUSR:	MVI A,00H OUT PORT A MVI B,0FH	;CLEAR CURSOR ;LOAD DATA PORT ;SET CHARACTER
CUSRI	:MOV A, B CALL DSPWLT DCR B JNZ CUSRI MOV A, B CALL DSPWLT MVI A, FFH OUT PORT B	;WRITE SUBRO ;DECREMENT C ;DIGIT 0? ; ; ;SET DATA FOR ;LOAD CONTROL
DISP:	LXI H, TABLE	;SET TABLE ADDRESS
DISP1	MOV A, M OUT PORT A MOV A, B CALL DSPWLT INX H INR B MVI A, 10H CMP B JNZ DISP1 HALT	;MOVE TABLE ADDRESS ;ACCUMULATOR ;LOAD DATA PORT ; ;LOAD ADDRESS ;CONTROL ;INCREMENT TABLE ;ADDRESS ;INCREMENT CURSOR ;SET # OF DIGITS ; ;16 CHARACTER ;END OF PROGRAM
DSPWLT	:ORI F0H OUT PORT C ANI 7FH OUT PORT C ORI F0H OUT PORT C RET	;SET CONTROL DATA ;LOAD CONTROL DATA ;SET WRITE BIT ;LOAD WRITE BIT ;ORI F0H ;LOAD CONTROL DATA
TABLE:	DB ;0C3H DB ;0C9H DB ;0D4H DB ;0D3H DB ;0C1H DB ;0D4H DB ;0CEH DB ;0C1H DB ;0C6H DB ;0A0H DB ;0D3H DB ;0D4H DB ;0C8H DB ;0C7H DB ;0C9H DB ;0CCH	

Figure 7. 16-digit parallel I/O system

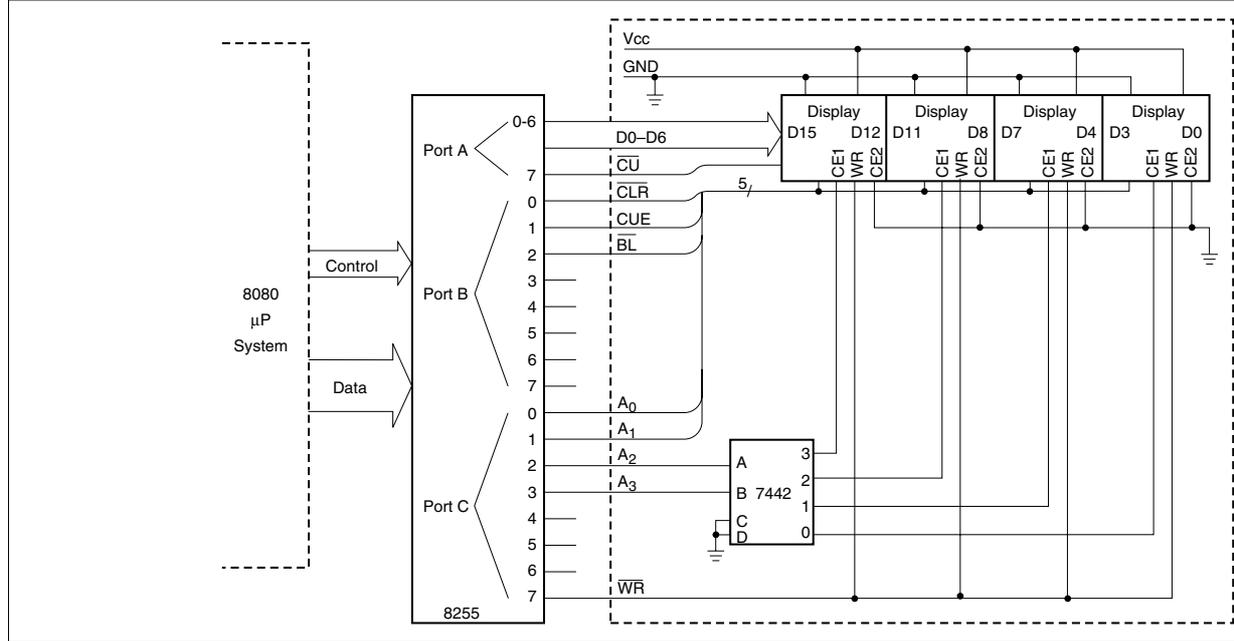


Figure 8. Mapped interface.

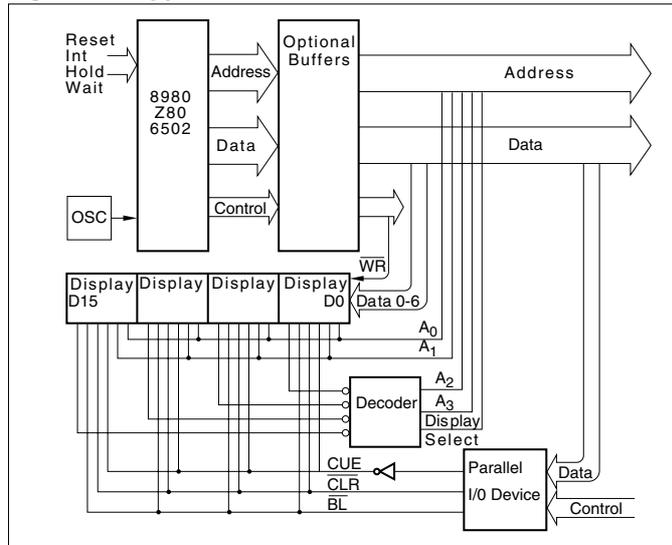


Figure 9. Interface with 6800 microprocessor

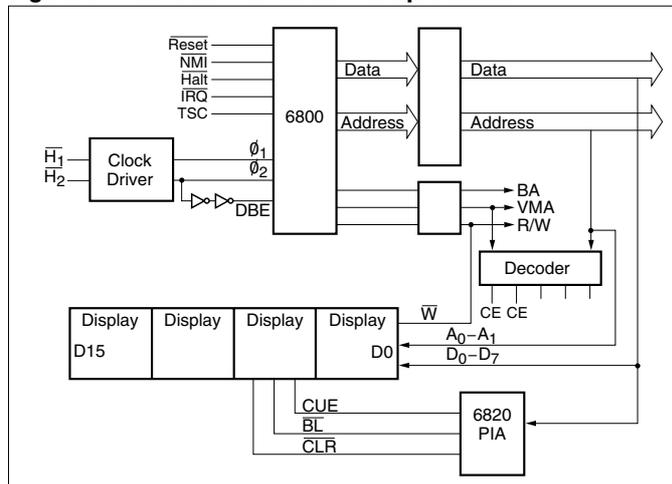


Figure 7 illustrates a 16 character display with a using the 8255 programmable peripheral interface. The following program will display a simple 16 c sage using this interface.

I/O or Memory Mapped Addressing

Some designers may wish to avoid the addition parallel I/O in their system. Structuring the address for the 3416 to look like a set of peripheral or ou (I/O mapped) or RAM's and ROM's (memory ma easy. Figure 8 shows the simplicity of interfacing processors, such as 8080, Z80 and 6502 as exampl

The interface with the 6800 microprocessor in F trates the need for designers to check the timing of the 3416 and the μP . The typical data output h 30 ns for DBE= $\emptyset 2$ timing; two inverters in the D added to increase the data output hold time for with the 50 ns minimum specification of the 34

Conclusion

Note that although other manufacturers' produ examples, this application note does not imply s endorsement, or recommendation or warranty of manufacturer's products by Infineon / OSRAM.

The interface schemes shown demonstrate the using the 3416 with microprocessors. The slight encountered with various microprocessors to int 3416 are similar to those encountered when usi RAMs. The techniques used in the examples w their generality, and any display of this family ar able in these examples. The user will undoubtedly schemes to optimize his particular system to its